

Please check that this question paper contains 9 questions and 2 printed pages within first ten minutes.

[Total No. of Questions: 09]

[Total No. of Pages: ..2....]

Uni. Roll No. ....

Program: B.Tech. (Batch 2018 onward)

Semester: 3

Name of Subject: Digital Circuits and Logic Design

Subject Code: ESIT-101

Paper ID: 16042

Time Allowed: 03 Hours

Max. Marks: 60

**NOTE:**

- 1) Parts A and B are compulsory
- 2) Part-C has Two Questions Q8 and Q9. Both are compulsory, but with internal choice
- 3) Any missing data may be assumed appropriately

**Part – A**

[Marks: 02 each]

**Q1.**

- a) What is De-Morgan's Theorem? (LOTS)
- b) What is decoder? Compare decoder and demultiplexer with suitable block diagram. (LOTS)
- c) Explain the term resolution and accuracy of A/D convertors. (LOTS)
- d) What is the difference between a latch and a flip flop. (LOTS)
- e) Perform Subtraction using 2's Complement:  $(101001)_2 - (001100)_2$  (HOTS)
- f) Add the following decimal numbers using BCD Addition and verify your result: 599 and 984 (HOTS)

**Part – B**

[Marks: 04 each]

**Q2.** Minimize the following expressions using Boolean algebra: (LOTS)

- 1)  $A'B.C + A.B'C + A.B.C' + ABC$
- 2)  $(ABC)'(A + C)(A + C')$

**Q3.** Implement full adder using two half adders and one OR gate. (LOTS)

**Q4.** What is Race around condition? How it can be avoided? Also discuss the working of Master Slave J-K Flip Flop. (LOTS)

**Q5.** Explain the working of 3-bit shift register. (HOTS)

**Q6.** Design 4-to-16 decoder with 2-to-4 decoder. (HOTS)

Q7. Draw the circuit of BCD adder and explain it. (HOTS)

**Part – C**

**[Marks: 12 each]**

Q8. Simplify the minterm expression for  $F : F(P,Q,R,S) = \sum (0,2,5,7,8,10,13,15)$  using K-Map. The minterms 2, 7, 8 and 13 are 'do not care' terms. (LOTS)

OR

What are universal gates and why they are called so? Implement AND, OR, NOT and XOR gates using NAND gates. (LOTS)

Q9. Design a combinational circuit to implement a 4-bit Binary to Gray code convertor. (HOTS)

OR

Differentiate between synchronous and asynchronous counters. Design 3-bit synchronous up counter using T flip flops. (HOTS)

\*\*\*\*\*